
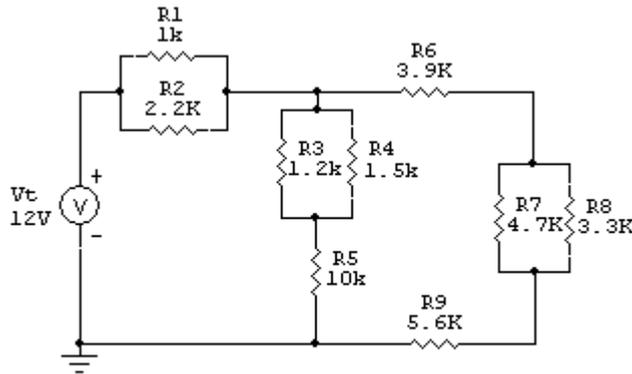


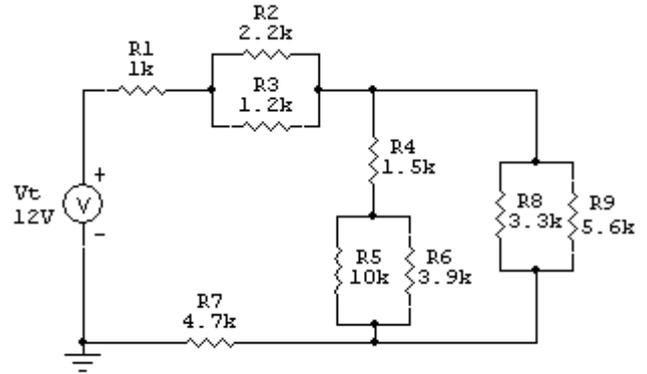


TALLER DIVISORES DE VOLTAJE Y CORRIENTE




CIRCUITO 1




CIRCUITO 2

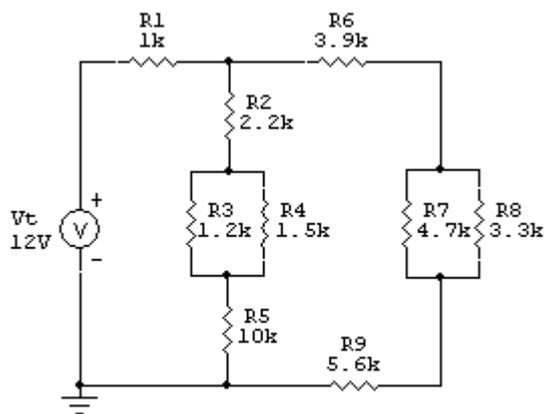


CIRCUITO 3

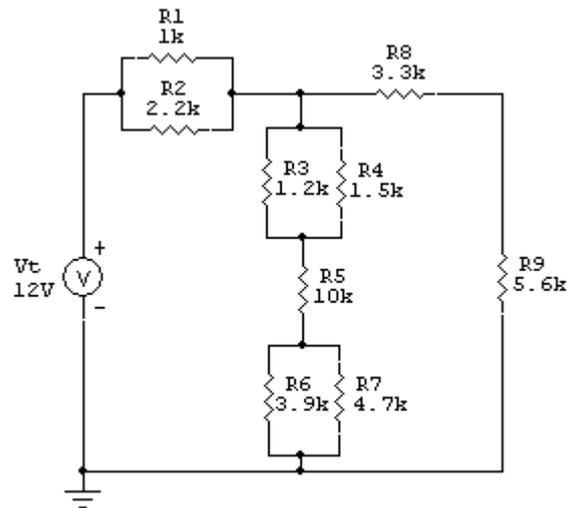


CIRCUITO 4

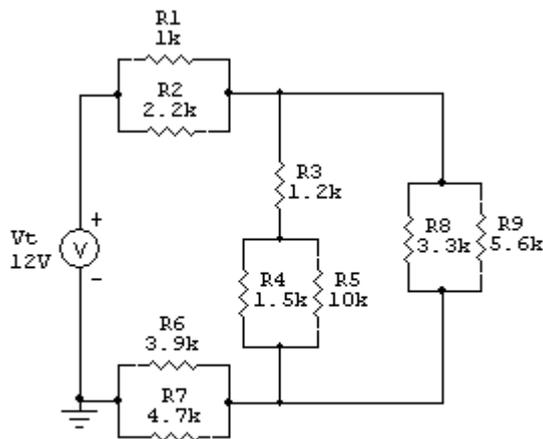


CIRCUITO 5

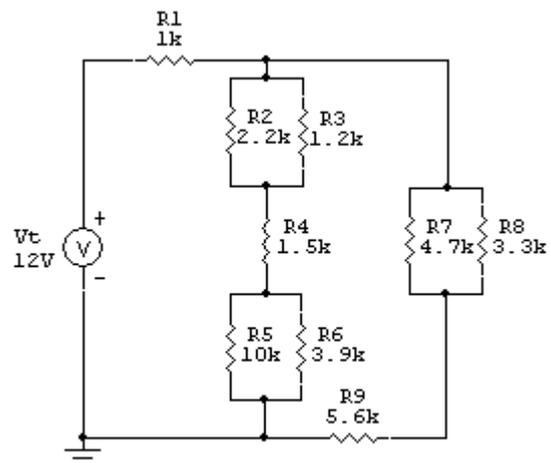


CIRCUITO 6

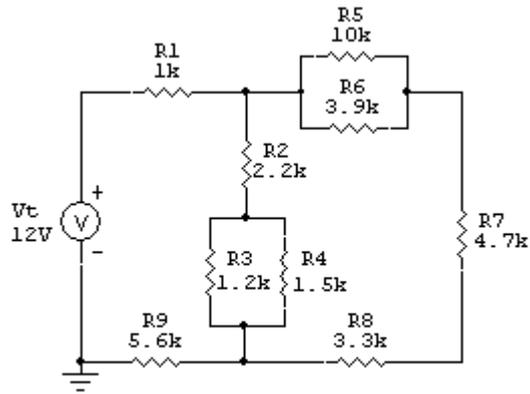


CIRCUITO 7

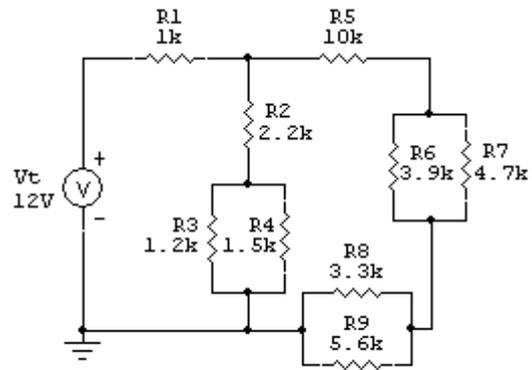

CIRCUITO 8

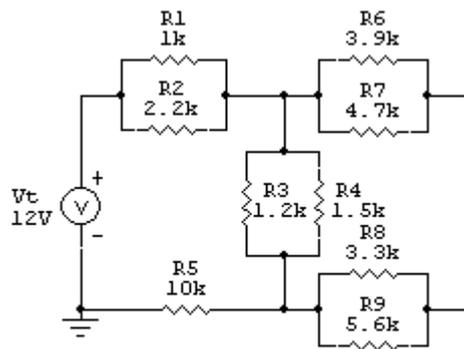

CIRCUITO 9

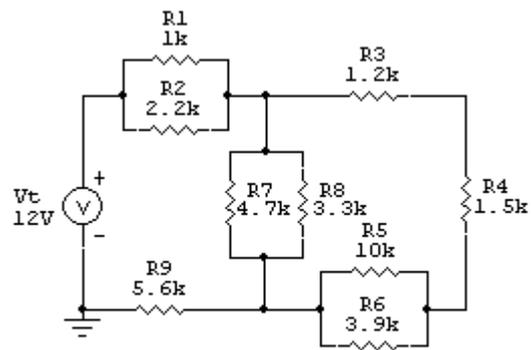

CIRCUITO 10